



Turun yliopisto  
University of Turku

**HDL Based Design**  
**ME620138**

# Libraries and Packages

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

*library*

```
entity half_adder is  
port(  
    x,y: in std_logic;  
    sum, carry: out std_logic);  
end half_adder;
```

*entity*

```
architecture myadder of half_adder is  
begin  
    sum <= x xor y;  
    carry <= x and y;  
end myadder;
```

*architecture*



# Concurrency

- Concurrent statements are evaluated at the same time; thus, the order of these statements doesn't matter
- Sequential/behavioural statements are executed in sequence

```
architecture dataflow of SR_flipflop is
begin
    gate_1 : q <= s_n nand q_n;
    gate_2 : q_n <= r_n nand q;
end architecture dataflow;
```

```
architecture checking of SR_flipflop is
begin
    set_reset : process (S, R) is
    begin
        assert S nand R;
        if S then
            Q <= '1';
        end if;
        if R then
            Q <= '0';
        end if;
    end process set_reset;
end architecture checking;
```




# Difference between Variables and Signals

- Variables are sequential statements
  - That is, they are used in processes
- Signals are concurrent statements
- **The value of a variable is updated immediately whereas the value of a signal is updated after a delay**
  - Very important to remember


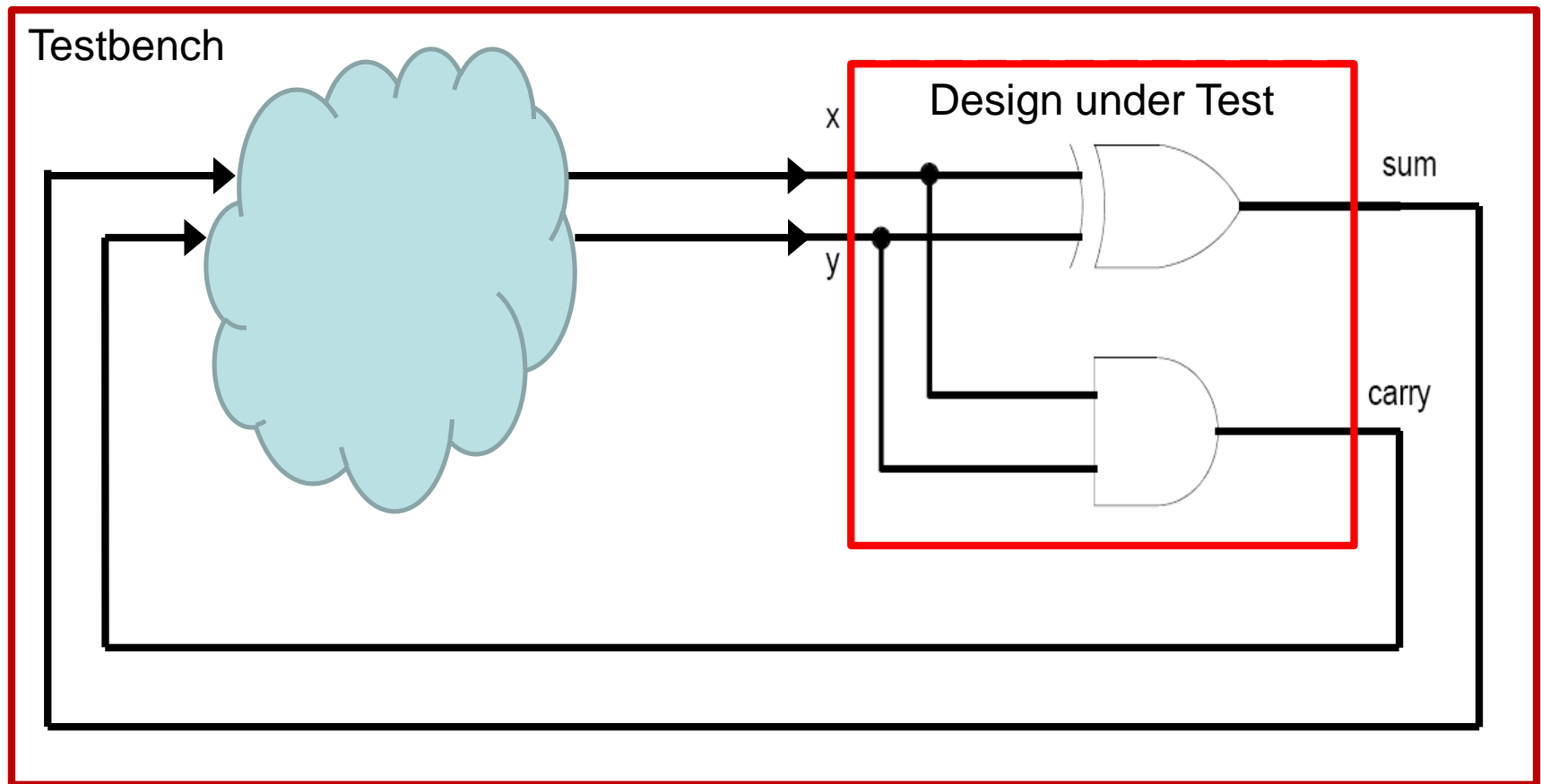
# Testbench

- Testbench generates input signals for Device under Test (DUT) and observes DUT's response



# SIMULATION



Turun yliopisto  
University of Turku

# Simulation Types

input



time driven



event driven




VHDL is  
event  
driven

cycle based




clock

 

Turun yliopisto  
University of Turku

# States of a Simulation Process

 


- **Suspended:** simulation process is not running or active
- **Active:** Simulation process is in the active processes queue waiting to be executed
- **Running:** Simulator is executing the simulation process





# Simulation

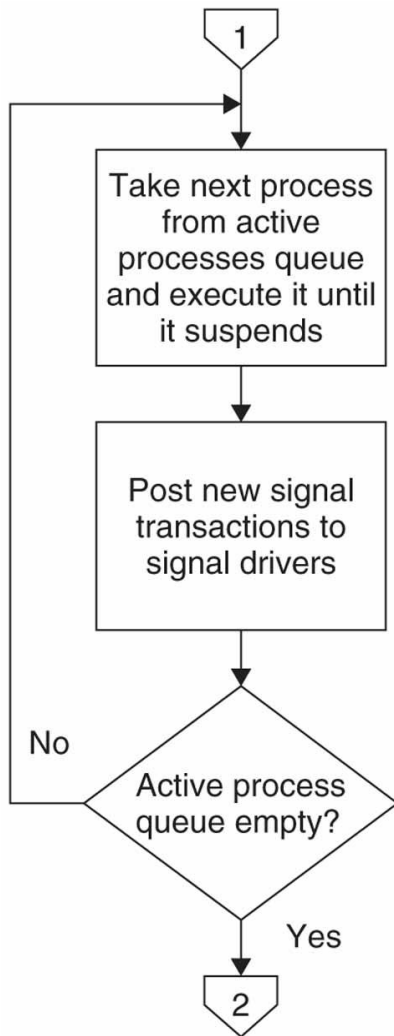

- Simulation cycle consists of *signal update* and *process execution* (the figure on the left) phases
- The order in which the active processes are executed is not important



# Simulation Cycle – in detail

1. The simulation time is first advanced to the next time at which a transaction on a signal has been scheduled
2. All the transactions scheduled for that time are performed
  - This may cause some events to occur on some signals
3. All processes that are sensitive to those events are resumed and are allowed to continue until they reach a wait statement and suspend
  - Again, the processes usually execute signal assignments to schedule further transactions on signals
4. When all the processes have suspended again, the simulation cycle is repeated
  - When there are no further scheduled transactions, the simulation ends



# Signals versus Variables

- Variable's value is updated immediately during the current simulation cycle
- Signal's value is not updated during the current simulation cycle
  - The new value will not take effect until the update phase of the next simulation cycle
  - Without any delay information the new value is updated after a *delta delay*



# Delta Delay

- The signal value does not change as soon as the signal assignment statement is executed
- The process does not see the effect of the assignment until the next time it resumes, even if this is at the same simulation time


```
s <= '1';
```

```
...
```

```
if s then ...
```



# Delta Cycle

 

To understand Delta Cycle, you should understand the simulation cycle in VHDL

signal update phase is followed by a process execution phase



# TIMING




Turun yliopisto  
University of Turku
 
# An Example Module

```
entity half_adder is  
port(  
    x,y: in std_logic;  
    sum, carry: out std_logic);  
end half_adder;
```

```
architecture myadder of half_adder is  
begin  
    sum <= x xor y;  
    carry <= x and y;  
end myadder;
```





# Timing

- To postpone the update of a signal value, use an **after** clause to define the time period

```
Dout <= not Din after 10 ns;
```

- The time period is added to current simulation time
- You can create a wave form using the **after** clause:


```
Dout <= '0' after 10 ns, '1' after 20 ns, '0' after 30 ns;
```


 
# An Example Module

```
entity half_adder is
port(
    x,y: in std_logic;
    sum, carry: out std_logic);
end half_adder;

architecture myadder of half_adder is
begin
    sum <= x xor y after 10 ns;
    carry <= x and y after 10 ns;
end myadder;
```



# Waiting

- Wait statement is used in processes to wait on signal changes or a time period

```
wait [sensitivity_clause] [condition_clause] [timeout_clause] ;
```

```
sensitivity_clause ::= on signal_name {, signal_name}
```

```
condition_clause ::= until boolean_expression
```

```
timeout_clause ::= for time_expression.
```

- With **on**, you can specify signal to which the process responds
- With **until**, you can stall the process until a condition is met
- With **for**, you can stall the process a time period



# Waiting

- Wait statement is used in processes to wait on signal changes or a time period

```
wait [sensitivity_clause] [condition_clause] [timeout clause] ;
```

```
sensitivity_clause ::= on signal_name {, signal_name}
```

```
condition_clause ::= until boolean_expression
```

```
timeout clause ::= for time_expression.
```

**wait on** clk **until** reset = '1';

**wait until** x **for** 10 ns;

**wait;**

*Wait on x, y until z='1' for 100 ns;*


The execution of the process is suspended for a maximum of 100 ns. **If an event occurs on x or y prior to 100 ns, the condition z is evaluated.** If z is true (that is z='1'), when the event on x or y occurs, the process will resume at that time; otherwise, suspension continues


 
# An Example Module

```
entity half_adder is
port(
    x,y: in std_logic;
    sum, carry: out std_logic);
end half_adder;

architecture myadder of half_adder is
begin
    process is
    begin
        sum <= x xor y after 10 ns;
        carry <= x and y after 10 ns;
    wait on x, y;
    end process;
end myadder;
```




# SYNCHRONOUS DESIGN




Turun yliopisto  
University of Turku

# Clock Signal

- Clock signal is a sequence of pulses

 

(a)

 

(b)



# Clocks

- Free running clock definitions:

```
signal clock : std_ulogic;  
...  
clock_gen : process is  
begin  
    clk <= '1';  
    wait for 10 ns;  
    clk <= '0';  
    wait for 10 ns;  
end process clock_gen;
```

```
signal clock : std_ulogic := '1';  
...  
clock <= not clock after 5ns;
```

- Limited number of clock cycles:

```
signal clock : std_ulogic;  
...  
process  
begin  
    for i in 1 to num_clockcycles loop  
        clock <= not clock;  
        wait for 10 ns;  
        clock <= not clock;  
        wait for 10 ns;  
    end loop;  
    wait;  
end process;
```





# Reset Signal

- Reset signal sets the system in a predefined state


```
signal clock : std_ulogic := '1';  
signal rst: std_logic;  
...  
rst <= '0', '1' after 10 ns, '0' after 100 ns;  
clock <= not clock after 5ns;
```



# LATCHES AND FLIP-FLOPS




# Signal Pulse

 

*Function table for a positive-level D latch.*


D	CLK	$Q_{t+1}$
0	0	$Q_t$
0	1	0
1	0	$Q_t$
1	1	1

 


*Function table for a positive-edge-triggered D flip-flop.*

D	CLK	$Q_{t+1}$
0	↑	0
1	↑	1
X	0	$Q_t$
X	1	$Q_t$

# D Latch

 

(a)

 


(b)


```
[process_label:] process (<clock_signal>, <input_signals>)  
  <declarations>  
begin  
  if <clock_level> then  
    <sequence_of_statements>  
  end if;  
end process [process_label];
```



# D Flip-flop

 

(a)

 

(b)


```
[process_label:] process (<clock_signal>)  
  <declarations>  
begin  
  if <clock_edge> then  
    <sequence_of_statements>  
  end if;  
end process [process_label];
```


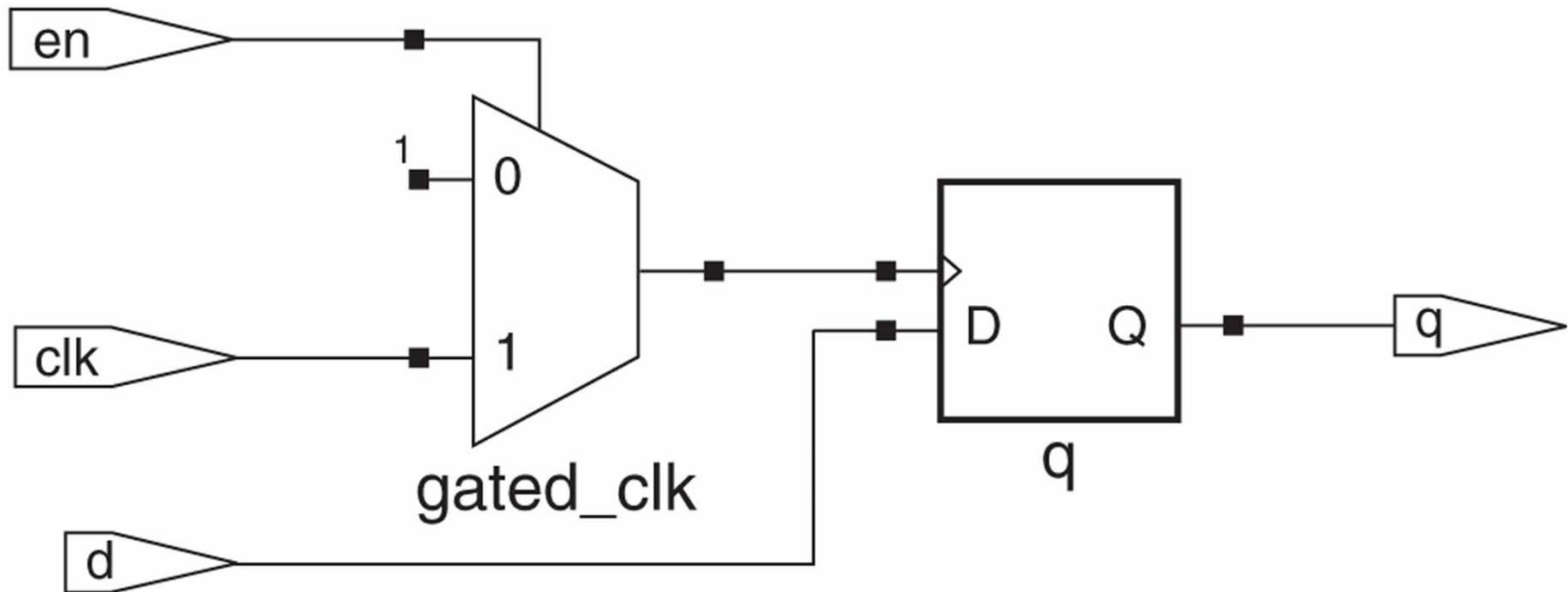
# Gated Flip-Flop

```
gated_clk <= clk when en = '1' else '1';
```


```
process (gated_clk) begin  
    if rising_edge(gated_clk) then  
        ...  
    end if;  
end process;
```


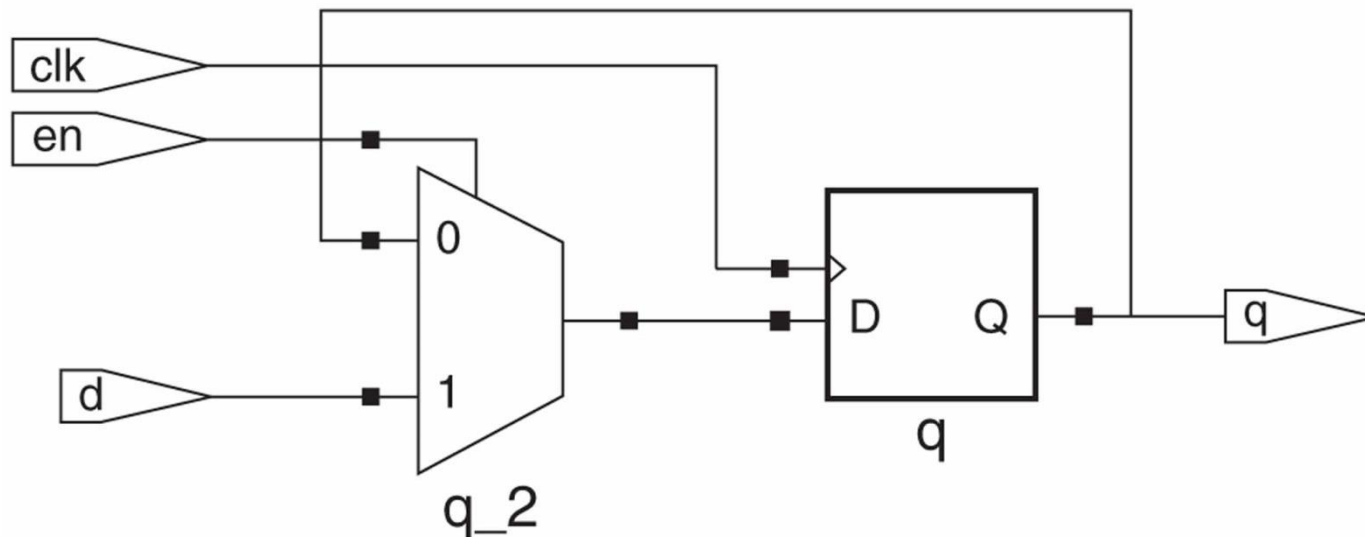
# Enabled Flip-Flop

```
process (clk) begin  
  if rising_edge(clk) then  
    if en = '1' then  
      q <= d ;  
    else  
      q <= q;  
    end if;  
  end if;  
end process;
```

```
process (clk) begin  
  if rising_edge(clk) then  
    if en = '1' then  
      q <= d ;  
    end if;  
  end if;  
end process;
```



# True and complement outputs for Flip-Flop

```
architecture dataflow is  
    signal qsig : std_logic;  
begin  
    process (clk) begin  
        if rising_edge(clk) then  
            qsig <= d ;  
        end if;  
    end if;  
    end process;  
    q <= qsig;  
    qnot <= not qsig;  
end architecture;
```





# Sync and Async Reset Signal

```
process (clk)
begin
    if rising_edge(clk) then
        if rst = '1' then
            dout <= 0;
        else
            dout <= d ;
        end if;
    end if;
end process;
```

```
process (clk,rst)
begin
    if rst = '1' then
        dout <= 0;
    elsif rising_edge(clk) then
        dout <= d ;
    end if;
end process;
```



# MEMORIES




Turun yliopisto  
University of Turku
 
# Register

```
if rising_edge(clk) then
  if rst= '0' then
    Q3 <= '0'
  else
    Q3 <= D3;
  end if;
end if;
```


How to change the code to create this register bank?


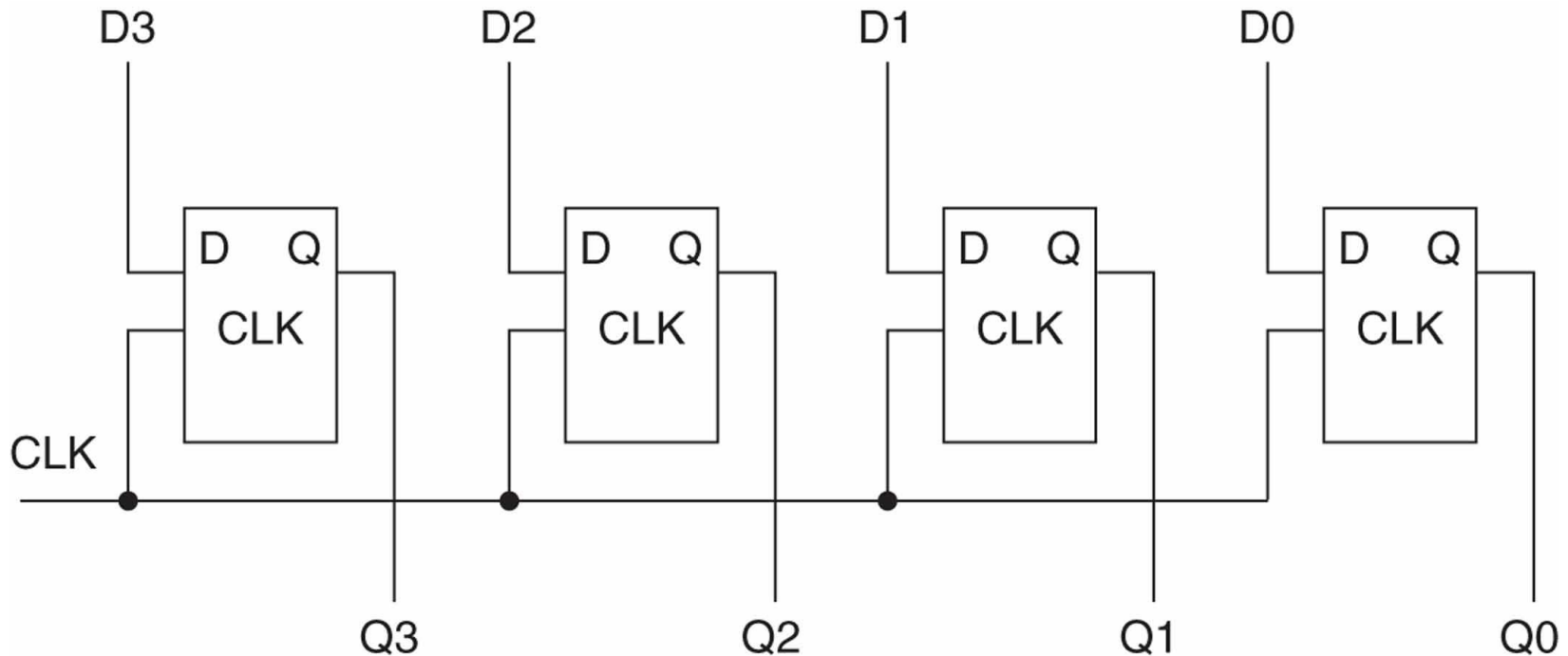
# Register


```
if rising_edge(clk) then
  if rst= '0' then
    Q3 <= '0'
  else
    Q3 <= D3;
  end if;
end if;
```

```
if rising_edge(clk) then
  if rst= '0' then
    Q <= "0000"
  else
    Q <= D;
  end if;
end if;
```


 
# Shift Register with Parallel Output

```
if rising_edge(clk) then
  if rst= '0' then
    SOUT <= "0000"
  else
    Q(0) <= Q(1);
    Q(1) <= Q(2);
    Q(2) <= Q(3);
    Q(3) <= SI;
  end if;
end if;
SOUT <= Q(0);
```




# Shift Register with Parallel Output

```
if rising_edge(clk) then
  If rst= '0' then
    SOUT <= "0000"
  else
    Q(0) <= Q(1);
    Q(1) <= Q(2);
    Q(2) <= Q(3);
    Q(3) <= SI;
  end if;
end if;
SOUT <= Q(0);
```

```
variable Qin : std_logic_vector(3 downto 0);

 if rising_edge(clk) then
  If rst= '0' then
    Qin := "0000"
  else
    Qin(0) := Qin(1);
    Qin(1) := Qin(2);
    Qin(2) := Qin(3);
    Qin(3) := SI;
  end if;
end if;
Q <= Qin;
SOUT <= Qin(0);
```



# Shift Register with Parallel Output

```
process (clk)
    variable Q : std_logic_vector(3 downto 0);
begin
    if rising_edge(clk) then
        if rst= '0' then
            Q := "0000"
        else
            Q := SI & Q(3 downto 1);
        end if;
        Qout <= Q;
    end if;
```

