




Turun yliopisto  
University of Turku

# **HDL Based Design**

## **ME620138**

# Hierarchical Design

- Top-down design

 

- Each module may itself be partitioned to further reduce its complexity



# GENERICS



Turun yliopisto  
University of Turku

# Generics

- Generics allow a design to be described so that its structure can be altered easily during the instantiation of the module

```
entity_declaration ::=
    entity identifier is
        [ generic ( generic_interface_list ) ; ]
        [ port ( port_interface_list ) ; ]
    end [ entity ] [ entity_simple_name ] ;


generic_interface_list ::=
[ constant ] identifier_list : [ in ] subtype_indication [ := static_expression ]
{ [ constant ] identifier_list : [ in ] subtype_indication [ := static_expression ] }
```


 
# Generic Example

```
entity half_adder is  
  generic (Tpd: time := 10 ns)  
  port( x,y: in std_logic;  
        sum, carry: out std_logic);  
end half_adder;
```

```
architecture myadder of half_adder is  
begin  
  sum <= x xor y after Tpd;  
  carry <= x and y after Tpd;  
end myadder;
```



- Generics are visible in the entity in which it is declared as well as in the corresponding architecture body



# Up Counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Counte3 is
port( clk: in std_logic;
      reset: in std_logic;
      count: out std_logic_vector(3 downto 0));
end Counte3;

architecture behavioural of Counte3 is
    signal counting: std_logic_vector(3 downto 0);
begin
    process (clk,reset)
    begin
        if reset = '0' then counting <= "0000";
        elsif (rising_edge(clk)) then counting <= counting + 1;
        end if;
    end process;
    count <= counting;
end behavioural;
```



# Up Counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Counte3 is
generic( w: natural := 4)
port( clk: in std_logic;
      reset: in std_logic;
      count: out std_logic_vector(w-1 downto 0));
end Counte3;

architecture behavioural of Counte3 is
  signal counting: std_logic_vector(w-1 downto 0);
begin
  process (clk,reset)
  begin
    if reset = '0' then counting <= (others => 0);
    elsif (rising_edge(clk)) then counting <= counting + 1;
    end if;
  end process;
  count <= counting;
end behavioural;
```

# Port Mapping with Generics

```
entity Counte3 is  
  generic( w: natural := 4)  
  port(  clk: in std_logic;  
        reset: in std_logic;  
        count: out std_logic_vector(w-1 downto 0));  
end Counte3;
```

```
c1:  entity work.counter (behavioural)  
      generic map (16)  
      port map (m_clk, m_reset, m_count);
```

```
c2:  entity work.counter (behavioural)  
      generic map (12)  
      port map (m_clk, m_reset, m_count);
```

```
c3:  entity work.counter (behavioural)  
      generic map (w => 16)  
      port map (m_clk, m_reset, m_count);
```





# Port Mapping with Generics (VHDL-2008)

```
entity Counte3 is  
  generic( type data_type)  
  port( clk: in std_logic;  
        reset: in std_logic;  
        count: out data_type);  
end Counte3;
```

```
c1: entity work.counter (behavioural)  
  generic map (data_type => std_logic_vector(3 downto 0))  
  port map (m_clk, m_reset, m_count);
```

```
generic ( type T; constant init_val : T );  
signal v : T := init_val;
```




# Port Mapping with Generics (VHDL-2008)
 
## NOTE

- To use types in generics requires one to be careful!
- For example, arithmetic operators are not defined for all the available types

```
entity counte3 is  
generic( type data_type )  
port(    . . .  
        Dout : out data_type);  
architecture  
    . . .  
    Dout <= Dout + 1;  
end architecture;
```





# GENERATE



Turun yliopisto  
University of Turku

# Generate

- With generate statement you can replicate a component during instantiation of the design

```
generate_label :  
    generation_scheme generate  
        [ { block_declarative_item }  
    begin ]  
        { concurrent_statement }  
    end generate [ generate_label ] ;
```

- Generate *label* is mandatory
- Generation scheme:
  - For loop
  - If statement



# Memory Element using Generate

```
entity NbitRegister is  
generic ( width : natural:=32 );  
port ( Din: in std_logic_vector( width-1 downto 0),  
      Dout: out std_logic_vector( width-1 downto 0),  
      clk, rst : std_logic);  
end NbitRegister;  
architecture generated is  
  component Dff is  
    port ( clk : in std_logic;  
          d : in std_logic;  
          q : out std_logic );  
  end component Dff;  
begin  
  generate_registers:  
  for i in (width-1) downto 0 generate  
    begin  
      dffn: component Dff  
        port map (Din(i), clk, rst, Dout(i) );  
    end generate generate_registers;  
end generated
```

} Concurrent  
statement



# Memory Element using Generate

**Entity** NbitFullAdder **is**

**generic** ( width : natural:=8);

**port**( a, b : **in** std\_logic\_vector (width-1 downto 0);

s : **out** std\_logic\_vector (width-1 downto 0);

cin : **in** std\_logic;

cout : **out** std\_logic );

**end** NbitFullAdder;

**architecture** dataflow **of** NbitFullAdder **is**

**signal** c : std\_logic\_vector (width-1 **downto** 0);

**begin**

array : **for** i **in** width-1 **downto** 0 **generate**

*-- remember component declarations*

**begin**

first : **if** i=0 **generate**

**begin**

cell : **component** full\_adder

**port map** (a(i), b(i), cin, s(i), c(i));

**end generate** first;

other : **if** i/=0 **generate**

**begin**

cell : **component** full\_adder

**port\_map** (a(i), b(i), c(i-1), s(i), c(i));

**end generate** other;

**end generate** array;

cout <= c(15);

**end architecture** dataflow;

# Memory Element using Generate

**Entity** NbitFullAdder **is**

**generic** ( width : natural:=8);

**port**( a, b : **in** std\_logic\_vector (width-1 downto 0);

s : **out** std\_logic\_vector (width-1 downto 0);

cin : **in** std\_logic;

cout : **out** std\_logic );

**end** NbitFullAdder;

**architecture** dataflow **of** NbitFullAdder **is**

**signal** c : std\_logic\_vector (width-1 **downto** 0);

*-- remember component declarations*

**begin**

array : **for** i **in** width-1 **downto** 0 **generate**

**begin**

first\_and\_others:

**if** i=0 **generate**

cell : **component** full\_adder

**port map** (a(i), b(i), cin, s(i), c(i));

**else generate**

cell : **component** full\_adder

**port\_map** (a(i), b(i), c(i-1), s(i), c(i))

**end generate** first\_and\_others;

**end generate** array;

cout <= c(15);

**end architecture** dataflow;





# Generate

- For generate
  - All elements are equivalent
  - discrete range must be specified
  - Loop cannot be terminated
- If generate
  - Conditional creation of elements
  - **elsif** or **else** alternatives are allowed only in VHDL-2008
- Case generate
  - Conditional creation of elements
  - Only available in VHDL-2008


Else and elsif  
Does not work with  
Questa 10.2 nor 10.4



# Exercise 6



# Exercise 6

 

## Exercise 6

$$\begin{array}{rcccc}
 & & m_1 & m_0 & \\
 & \times & q_1 & q_0 & \\
 \hline
 & & m_0 q_1 & m_0 q_0 & \\
 + & m_1 q_1 & m_1 q_0 & & \\
 \hline
 & p_3 & p_2 & p_1 & p_0
 \end{array}$$

				1	0	1	1
			x	1	1	0	1
				1	0	1	1
	+		0	0	0	0	
			0 <sup>1)</sup>	1	0	1	1
	+	1	0	1	1		
	1)	1 <sup>1)</sup>	1	0	1	1	1
+	1	0	1	1			
1	0	0	0	1	1	1	1

(11) Kerrottava (multiplicand)

(13) Kertoja (multiplier)

(143) Tulo (product)